
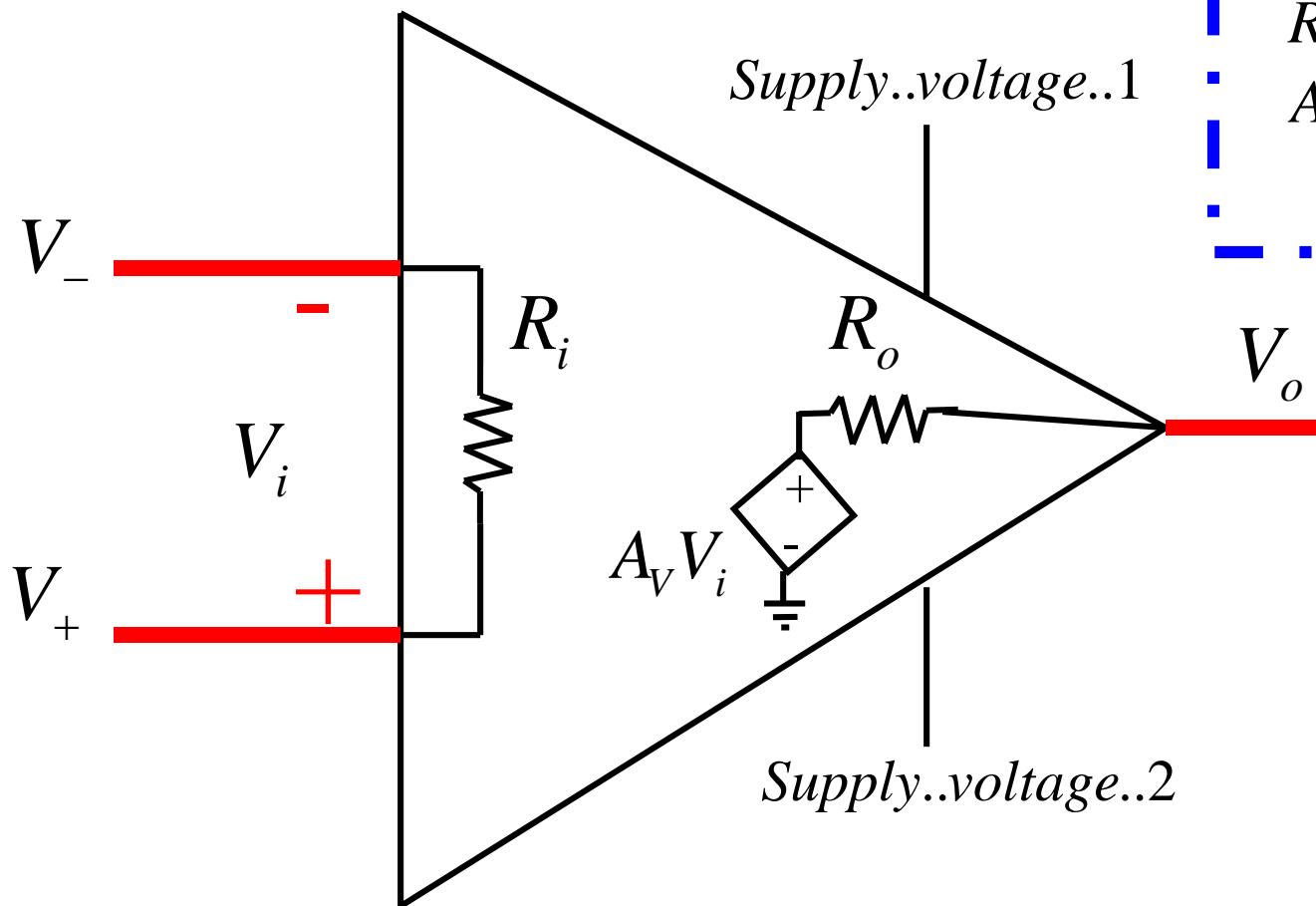


Operational Amplifier

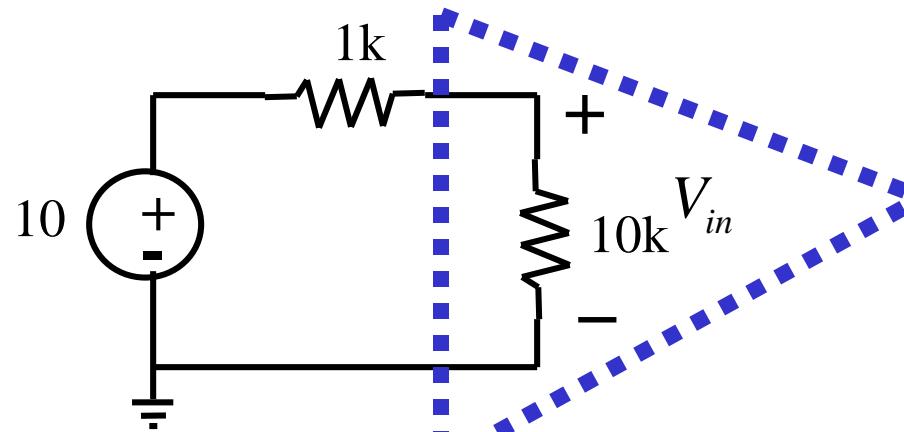


- $R_i \rightarrow \infty$
- $R_o \rightarrow 0$
- $A_V \rightarrow \infty$


$R_i \rightarrow \infty$


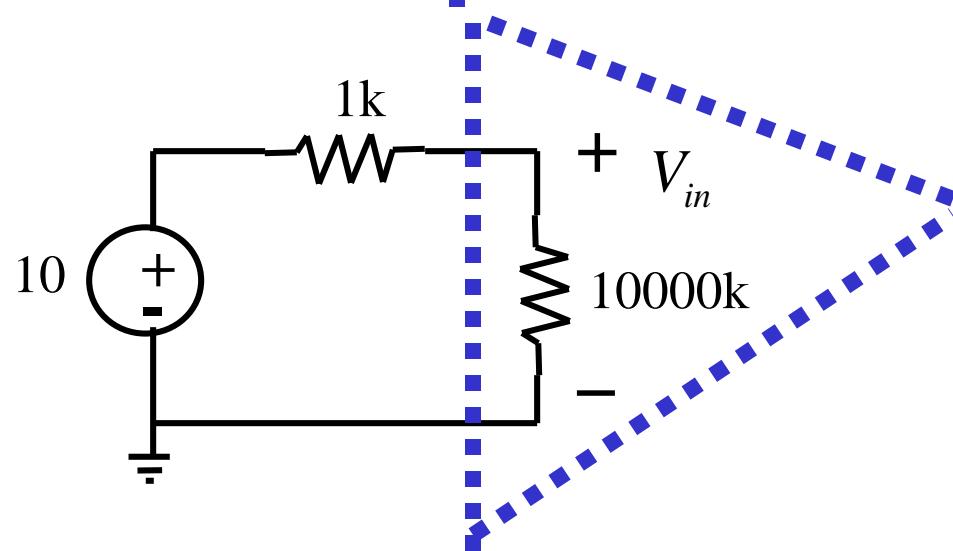
$$V_{in} = \frac{10k}{10k + 1k} 10 \\ = 9.09v$$



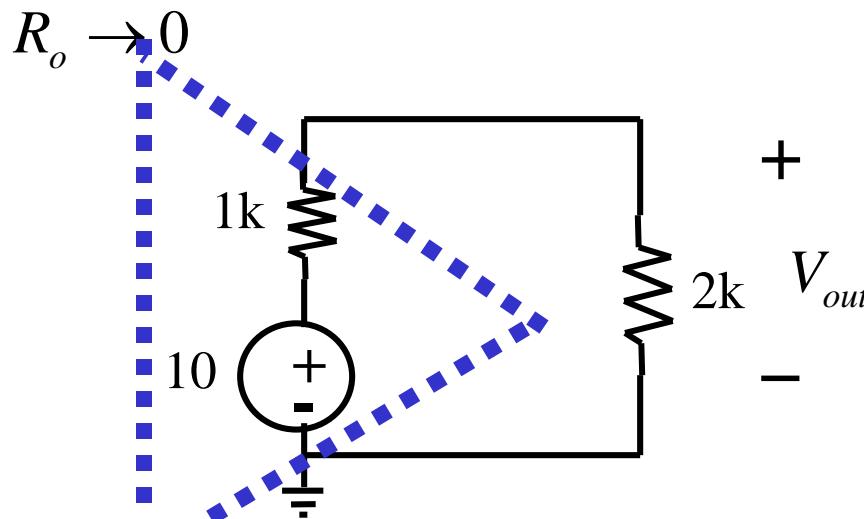
$$V_{in} = \frac{10000k}{10000k + 1k} 10 \\ = 9.999v$$



$$V_{out} = \frac{2k}{1k + 2k} 10$$


$$= 6.6667v$$

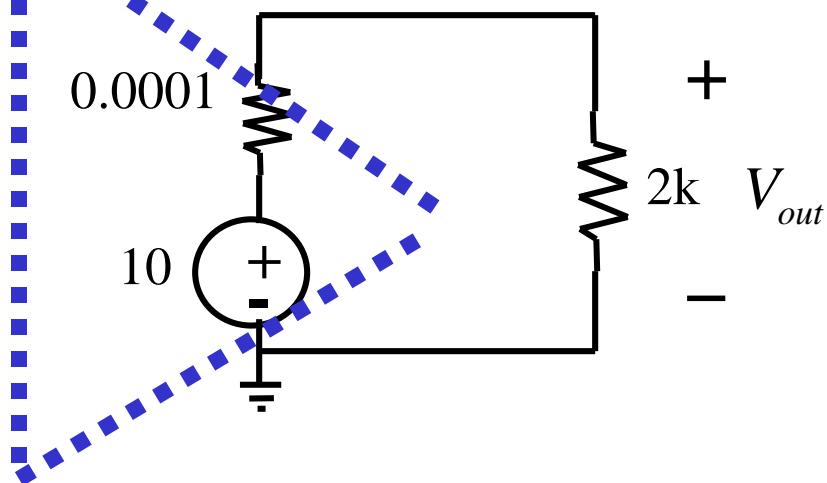

$$V_{out} = \frac{2k}{0.0001 + 2k} 10$$

$$\approx 10v$$



Ideal Op. Amp

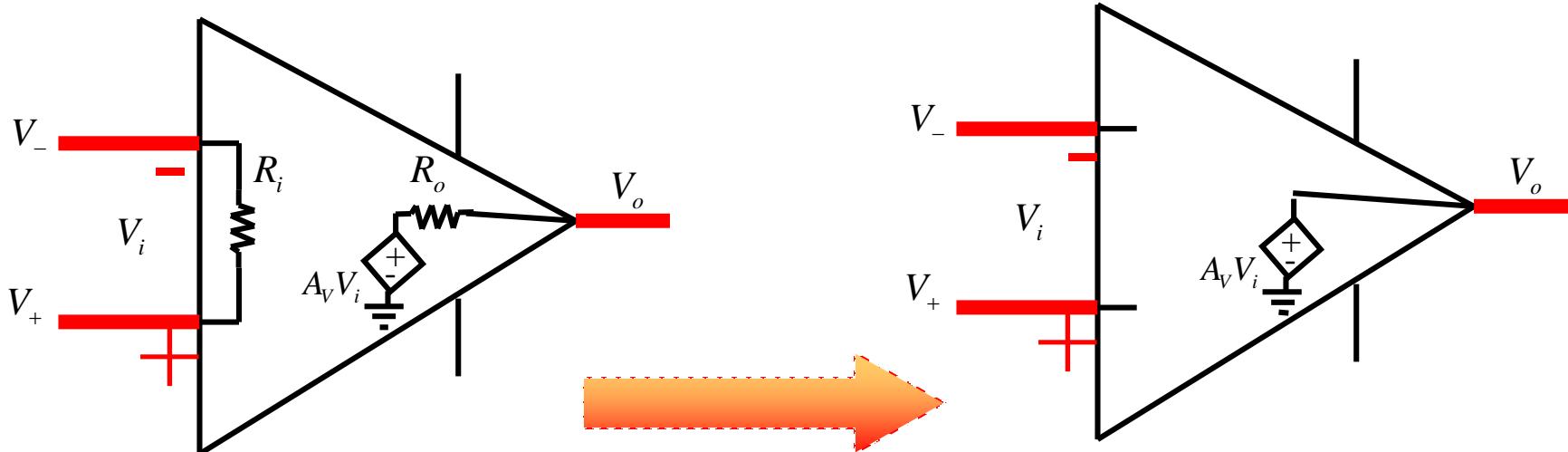

$$R_i \rightarrow \infty \quad \xrightarrow{\text{ }} \quad I_i \approx 0$$

$$R_o \rightarrow 0 \quad \xrightarrow{\text{ }} \quad \frac{V_o}{V_i} = A_V \Rightarrow V_i = \frac{V_o}{A_V} \Rightarrow V_+ - V_- = \frac{V_o}{A_V}$$

$$A_V \rightarrow \infty \quad \xrightarrow{\text{ }} \quad V_+ - V_- = \frac{V_o}{A_V} \Rightarrow V_+ \approx V_-$$

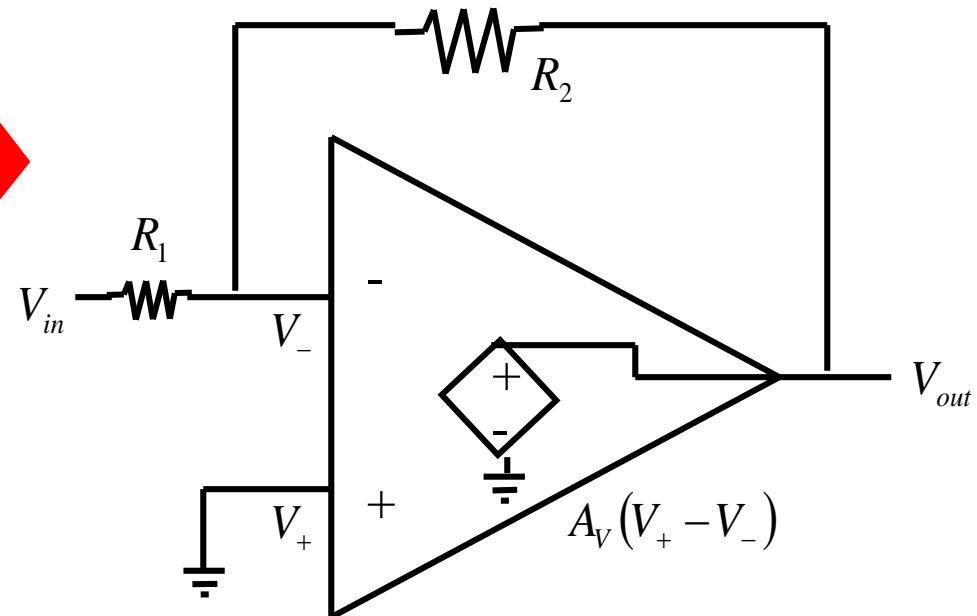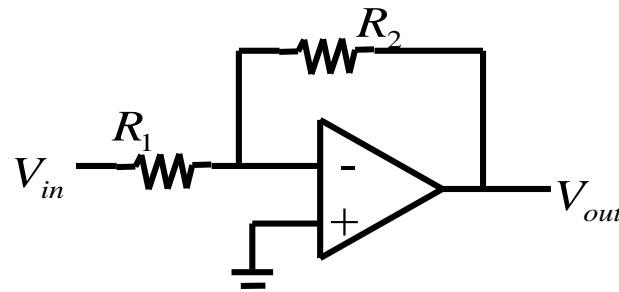
Ex. 3

$$K_F = ?$$

$$V_{out} = A_V(V_+ - V_-)$$


$$V_+ = 0$$
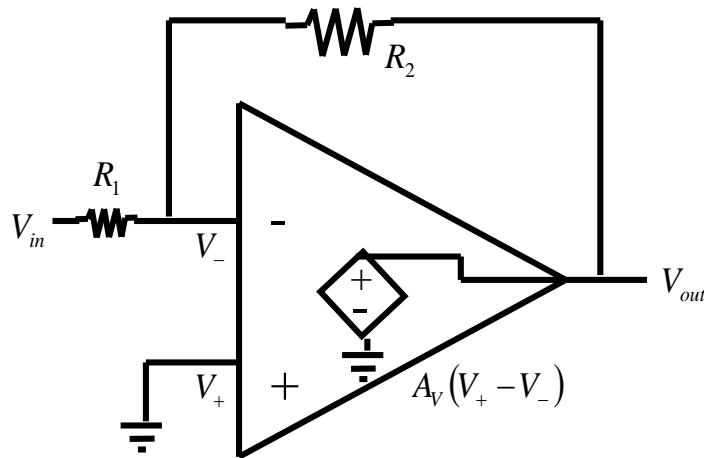
$$\frac{V_{in} - V_-}{R_1} + \frac{V_{out} - V_-}{R_2} = 0$$




$$K_F = \frac{V_{out}}{V_{in}} = -\frac{1 - \left[\frac{R_1}{R_1 + R_2} \right]}{\frac{1}{A_V} + \left[\frac{R_1}{R_1 + R_2} \right]}$$

@ $A_V \rightarrow \infty$

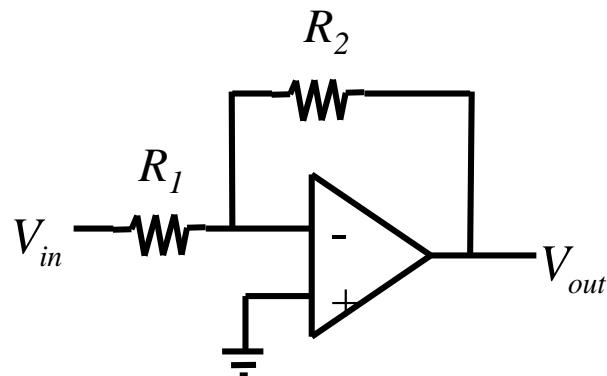


$$K_F = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

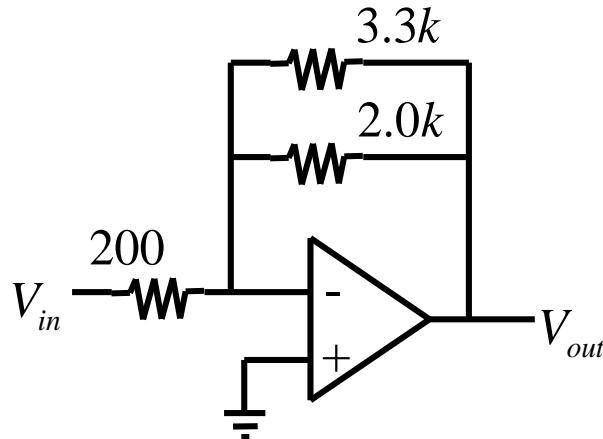Ex. 4

$$A_F = ?$$

\downarrow

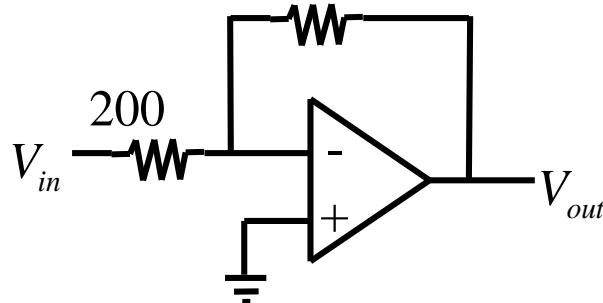
$$\frac{1}{\frac{1}{3.3k} + \frac{1}{2.0k}} = 1.245k$$



$$\begin{aligned} A_F &= \frac{V_{out}}{V_{in}} \\ &= -\frac{1.245k}{200} \end{aligned}$$

$$A_F = -6.23$$


Ex.

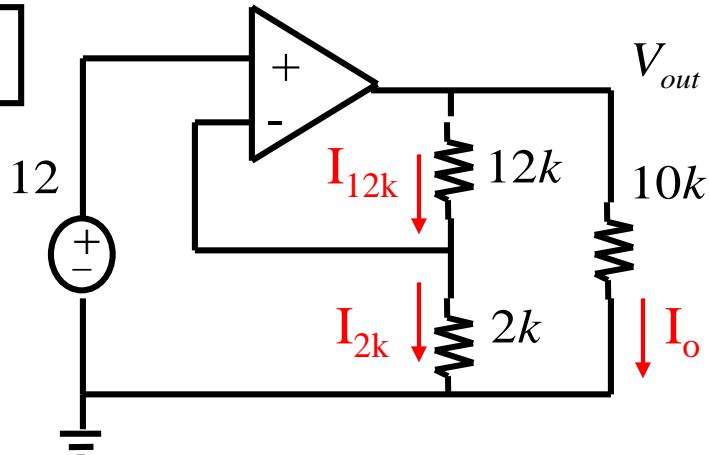


$$I_O = ?$$

$$V_+ = V_- = 12$$

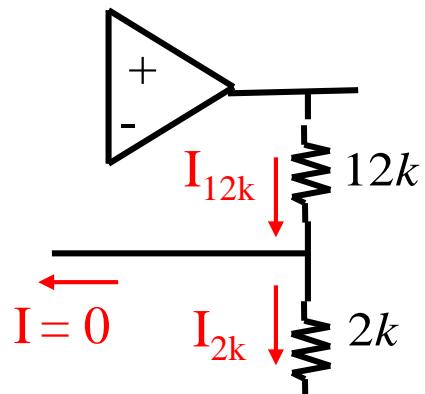
$$\begin{aligned} I_{2k} &= \frac{V_-}{2k} \\ &= \frac{V_+}{2k} \\ &= \frac{12}{2k} \\ &= 6mA \end{aligned}$$



$$I_{12k} = I_{2k} = 6mA$$

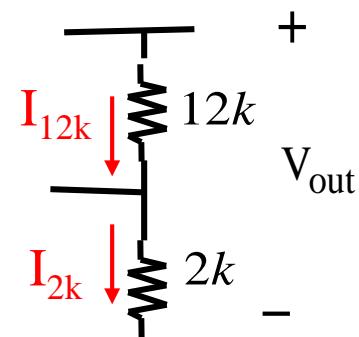

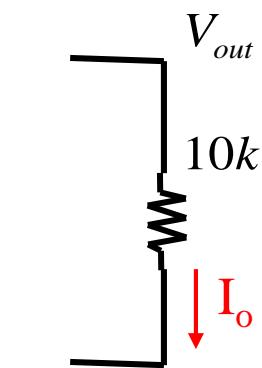
$$\begin{aligned} V_{out} &= (12k + 2k) * 6m \\ &= 84V \end{aligned}$$




$$I_o = \frac{84}{10k} = 8.4mA$$

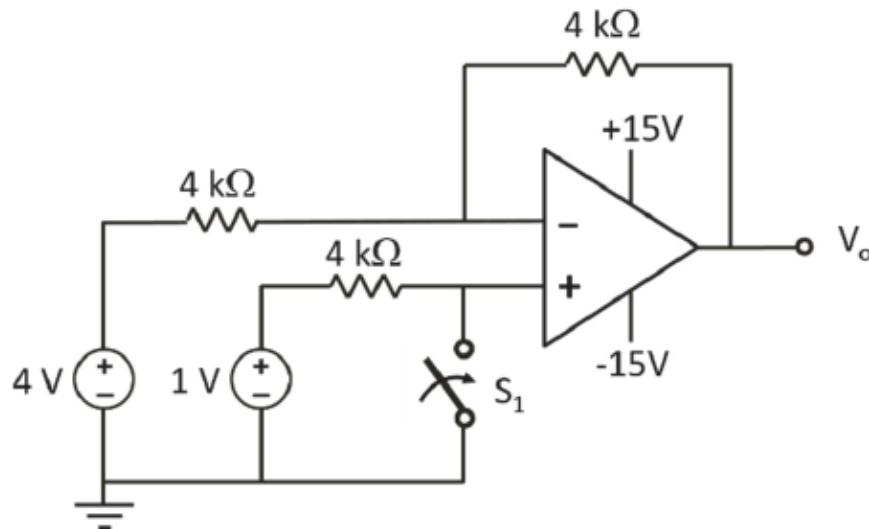Assuming ideal op amp, find the voltage V_o , (a) when the switch, S_1 , is open, and (b) when S_1 is closed.



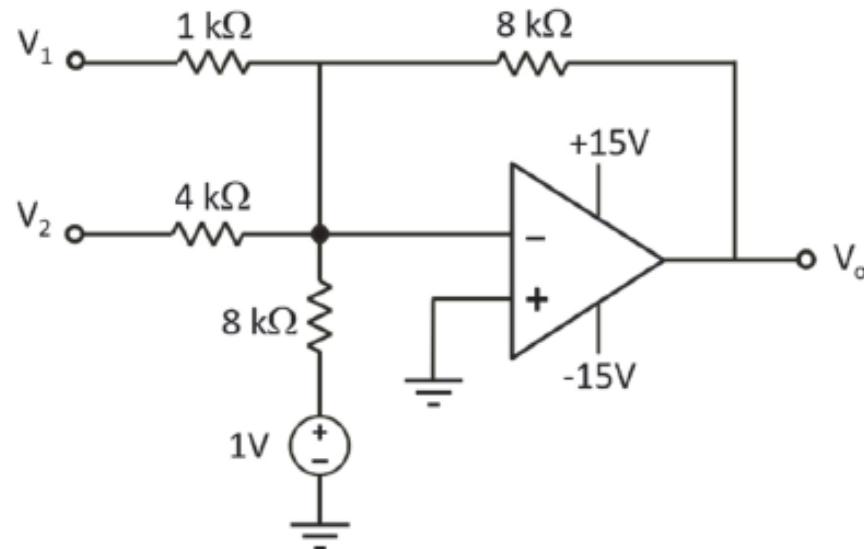Assuming ideal op amp, determine an expression for the output voltage, V_o , in terms of the inputs, V_1 , and V_2 .



Find V_o and I_s assuming ideal op amps.

